

Note: Attempt all the sections as per instruction.

SECTION-A

(Very Short Answer Questions)

Note: Attempt all Five questions. Each question carries 3 (Three) marks. Very short answer is required not exceeding 75 words. (3×5=15)

- 1) What are need of NAND and why this is called as universal gates?
- 2) What are adders? And how full adders are constructed from using two half-adders?
- 3) What is multiplexer? Also explain 8×1 multiplexer using 4×1 .
- 4) What is main memory and explain the EPROM?
- 5) What is flip-flop? Explain the RS flip-flop using NAND gate.

SECTION-B

(Short Answer Questions)

Note: Attempt any Two questions out of the following 3 (Three) questions. Each question carries 7.5 marks. Short answer is required not exceeding 200 words. (7.5×2=15)

- 6) What is Master-Slave flip-flop?
- 7) Writes short notes on RAM and CD-ROM?
- 8) Explain the 2D and $2\frac{1}{2}$ D Chip Organization? And compare both of them?

SECTION-C

(Detailed Answer Questions)

Note: Attempt any Three questions out of the following Five questions. Each question carries 15 marks. Answer is required in detail. (3×15=45)

- 9) What is shift register and explain its types?
- 10) Simplify the following Boolean function using Sum-of-Product form, by Karnaugh's map : $F(A, B, C, D) = \sum (0, 2, 3, 5, 7, 8, 10, 13, 15)$
- 11) Explain the general register organization and differentiate between synchronous and asynchronous counter?
- 12) What is cache memory? And explain various mapping functions and cache memory read and write operation?
- 13) What is virtual memory? Explain various page replacement policies with example?